

# Multi-Cycle RISC-V Processor Implementation Report

Beyrem Hadj Fredj

December 15, 2025

**Repository Link:** <https://github.com/BeyremHF/RISC-V-Processor-in-Verilog/tree/RV-MC>

## 1 Implementation Overview

This report documents the implementation of a multi-cycle RISC-V processor (RV32I subset) that executes instructions over multiple clock cycles using a Finite State Machine (FSM) controller.

### 1.1 Implemented Instructions

The processor supports 24 RISC-V instructions across 6 instruction types:

- **R-type:** ADD, SUB, AND, OR, XOR, SLT, SLTU, SLL, SRL, SRA
- **I-type (arithmetic):** ADDI, ANDI, ORI, XORI, SLTI, SLTIU, SLLI, SRLI, SRAI
- **Load:** LW
- **Store:** SW
- **Branch:** BEQ
- **Jump:** JAL
- **Upper Immediate:** LUI

### 1.2 Test Results

The processor was validated using a comprehensive test program covering all 24 instructions; 38/38 tests passed.

## 2 Architectural Questions

- **Question 1:** In Figure 1, some registers have write enable (en) while some do not. Explain why en is necessary or not.  
Some registers depend on the clock cycle to be updated, and some only get updated conditionally, according to the write enable signal.

- **Question 2: Why is the output of the sign extender not registered?**

The sign extender is purely combinational logic. Its output is used immediately in the same cycle or registered downstream by other registers (like being fed to ALU through MUXes).

- **Question 3: Where is the slowest datapath (critical path) between two registers, given the delays of the components?**

The slowest (critical) path between two registers is Memory Read: Register clk-Q (40ps) + Multiplexer (30ps) + Mem Read (200ps) + Multiplexer (30ps) = 300ps.

- **Question 4: How does a multicycle architecture allow the clock period to be shorter than in a single-cycle one? What is the benefit?**

The clock period is shorter because in the Multi-Cycle architecture, the clock period follows the shortest cycle, and not the shortest instruction. This way, we can use a higher frequency.

- **Question 5: Why might a multicycle design be easier (or harder) to extend with new instructions compared to a single-cycle design?**

Extending the CPU design with more instructions can be both hard and easy. It can be easy, where the FSM can be extended with new states for complex instructions without affecting the clock period. And it can be more challenging, as we must carefully design state transitions and ensure that control signals are correct across multiple cycles.

- **Question 6: Briefly describe the bug you have encountered.**

One particular bug I encountered is that the ALU decoder didn't distinguish R-type vs I-type, breaking negative immediates. Fixed by differentiating the instruction type using the "alu\_op" 2-bit signal: 10 = R-type only, while 11 = I-type only.

## 3 FSM Controller Design

The multi-cycle controller is implemented as a 12-state FSM that orchestrates instruction execution across multiple clock cycles.

### 3.1 State Descriptions

State	Description
S0 (FETCH)	Fetch instruction from memory using PC, compute PC+4
S1 (DECODE)	Decode instruction, read register file
S2 (COMPUTE)	Execute ALU operation for address/target calculation
S3 (MEM_ADDR)	Compute memory address for LW/SW
S4 (MEM_READ)	Read data from memory (LW only)
S5 (MEM_WB)	Write memory data to register file
S6 (MEM_WRITE)	Write data to memory (SW only)
S7 (EXEC_R)	Execute R-type ALU operation
S8 (EXEC_I)	Execute I-type ALU operation
S9 (ALUWB)	Write ALU result to register file
S10 (JAL)	Write PC+4 to register file for JAL
S11 (LUI)	Write immediate to register file for LUI

Table 1: FSM State Descriptions

## 3.2 FSM State Diagram

 


Figure 1: Complete FSM State Diagram with Control Signals

## 4 Control Signal Tables

### 4.1 Main Decoder Control Signals

State	we_pc	we_ir	we_rf	we_mem	sel_mem_addr	sel_alu_src_a	sel_alu_src_b	sel_result
S0	1	1	0	0	0	00	10	XX
S1	0	0	0	0	X	XX	XX	XX
S2	0	0	0	0	X	01	01	XX
S3	0	0	0	0	X	10	01	XX
S4	0	0	0	0	1	XX	XX	XX
S5	0	0	1	0	X	XX	XX	01
S6	0	0	0	1	1	XX	XX	XX
S7	0	0	0	0	X	10	00	XX
S8	0	0	0	0	X	10	01	XX
S9	0	0	1	0	X	XX	XX	00
S10	1	0	1	0	X	XX	XX	10
S11	0	0	1	0	X	XX	XX	11

Table 2: Control Signals per State (X = don't care)

## 5 Performance Analysis

### 5.1 Cycle Counts per Instruction Type

Instruction Type	Cycles
LW (Load Word)	5
SW (Store Word)	4
R-type	4
I-type (arithmetic)	4
BEQ (Branch)	4
JAL (Jump and Link)	4
LUI (Load Upper Imm)	3

Table 3: Clock Cycles per Instruction Type

### 5.2 Execution Paths per Instruction Type

Instruction Type	State Sequence
LW (Load Word)	S0 → S1 → S3 → S4 → S5
SW (Store Word)	S0 → S1 → S3 → S6
R-type	S0 → S1 → S7 → S9
I-type (arithmetic)	S0 → S1 → S8 → S9
BEQ (Branch)	S0 → S1 → S2 → S0
JAL (Jump)	S0 → S1 → S2 → S10 → S0
LUI	S0 → S1 → S11

Table 4: FSM State Sequences for Each Instruction Type

### 5.3 Average CPI Calculation

Based on the test program execution:

- **Total Instructions:** 38
- **Total Cycles:** 152
- **Average CPI:**  $152 / 38 = 4.00$

#### Instruction Breakdown:

- R-type: 13 instructions  $\times$  4 cycles = 52 cycles
- I-type: 17 instructions  $\times$  4 cycles = 68 cycles
- LW: 1 instruction  $\times$  5 cycles = 5 cycles
- SW: 4 instructions  $\times$  4 cycles = 16 cycles
- BEQ: 1 instruction  $\times$  4 cycles = 4 cycles
- JAL: 1 instruction  $\times$  4 cycles = 4 cycles
- LUI: 1 instruction  $\times$  3 cycles = 3 cycles

